

# **EECS 4612 - Digital VLSI**

Term Project: Design of 32-bit ALU

Abdulbasit Ali



# Introduction

Modern digital systems rely heavily on the Arithmetic Logic Unit (ALU), a core computational component responsible for executing arithmetic, logic, and shift operations. As the backbone of processors, microcontrollers, and custom ASICs, the ALU plays a vital role in determining system performance, functionality, and scalability. Developing a robust, modular, and physically realizable ALU is therefore essential in contemporary VLSI and system-on-chip (SoC) design workflows.

This project focuses on the complete design, verification, and physical implementation of a scalable ALU system, beginning with a fully functional 1-bit slice and extending it hierarchically into a 32-bit datapath. The 1-bit ALU was designed to support a comprehensive set of operations, including:

- **Arithmetic operations:** transfer, addition, addition with carry, subtraction, subtraction with borrow, increment, and decrement.
- **Logic operations:** AND, OR, XOR, and NOT.
- **Shift operations:** logical shift left and logical shift right.

The initial 1-bit unit was implemented using structural Verilog and thoroughly verified through self-checking testbenches. Once validated, the slice was instantiated thirty-two times to construct two complete 32-bit ALU variants:

1. A **structural modular design** composed of interconnected 1-bit slices.
2. A **behavioral RTL design** implementing the same functionality at a higher abstraction level.

Both implementations underwent full functional verification followed by synthesis, place-and-route, and physical design checks (DRC and LVS) using the Cadence Virtuoso and Innovus toolchains. This ensured that the final layouts adhered to foundry design rules and were ready for fabrication.

Post-layout timing and area analysis revealed key differences between the two methodologies. The behavioral ALU achieved the highest performance, reaching approximately **16.39 MHz**, compared to **11.61 MHz** for the structural modular design. The behavioral version also occupied substantially less silicon area - approximately **975.726  $\mu\text{m}^2$** , versus **1451.106  $\mu\text{m}^2$**  for the structural implementation. These improvements are attributed to cleaner routing, reduced logic depth, and greater synthesis optimization achievable in behavioral RTL descriptions.

Given its superior timing and area efficiency, the behavioral ALU was selected for full-chip integration. The design was incorporated into a top-level layout containing a pre-designed pad frame, with all necessary VDD, VSS, and signal pad connections routed across multiple metal layers. The resulting layout was exported in GDSII format, completing a fabrication-ready physical design.

Overall, this project demonstrates the development of a hierarchical ALU system from bit-level logic to chip-level implementation. It highlights the full digital design workflow, including modular design, verification, synthesis, physical implementation, and layout integration, and illustrates practical considerations such as timing closure, area optimization, and pad frame connectivity. The successful realization of the 32-bit ALU emphasizes both technical proficiency and readiness for industry-standard VLSI development processes.

## Objectives

This project is divided into 2 main parts. The first is targeted towards the ASIC flow for a 1-bit ALU using a modular approach. After the full flow is completed, we move onto the second stage.

The second stage is creating a 32-bit ALU using the modular approach which takes the 1 bit-alu and replicates it 32 times. The second approach is the behavioral design where it is simply just a 32-bit wide ALU. The more efficient chip is then selected to become the final design, after connecting it to a padframe given on eClass. The full ASIC flow for this ALU is seen below. With the way I have structured this report, I start by creating the 1-bit ALU, followed by both 32-bit ALUs.

# Part 1: 1 Bit ALU

## 1-bit ALU Elements


According to the manual given to us, the required components of this ALU included the following:

- 1-bit arithmetic circuit
  - 4x1 Mux
  - Full adder
- 1 bit logic circuit
  - 4x1 Mux
- MUX

With all those things combined, you can then build the ALU. The approach I took was to have a modular structure. I created a top-level file for the 1-bit ALU, with separate instantiations for the 1-bit arithmetic circuit (consisting of the mux and FA), along with the 1-bit logic circuit and another 4-1 mux. Designing these components and verifying them is critical to having this entire project function. Without a working 1-bit ALU, you won't be able to create any of the 32-bit ALUs since these sub-modules are used later. Below is the full flow.

 
4-1 Mux Design:

This MUX is used to enable the selection between data inputs based on other signals. The mux implements using AND OR NOT gates. There are 2 control signals S0 and S1. The table below shows which signals result in which outputs.



S0	S1	X (input)	Y (output)
0	0	A	A
1	0	B	B
0	1	C	C
1	1	D	D

Simulated Waveform for Mux:

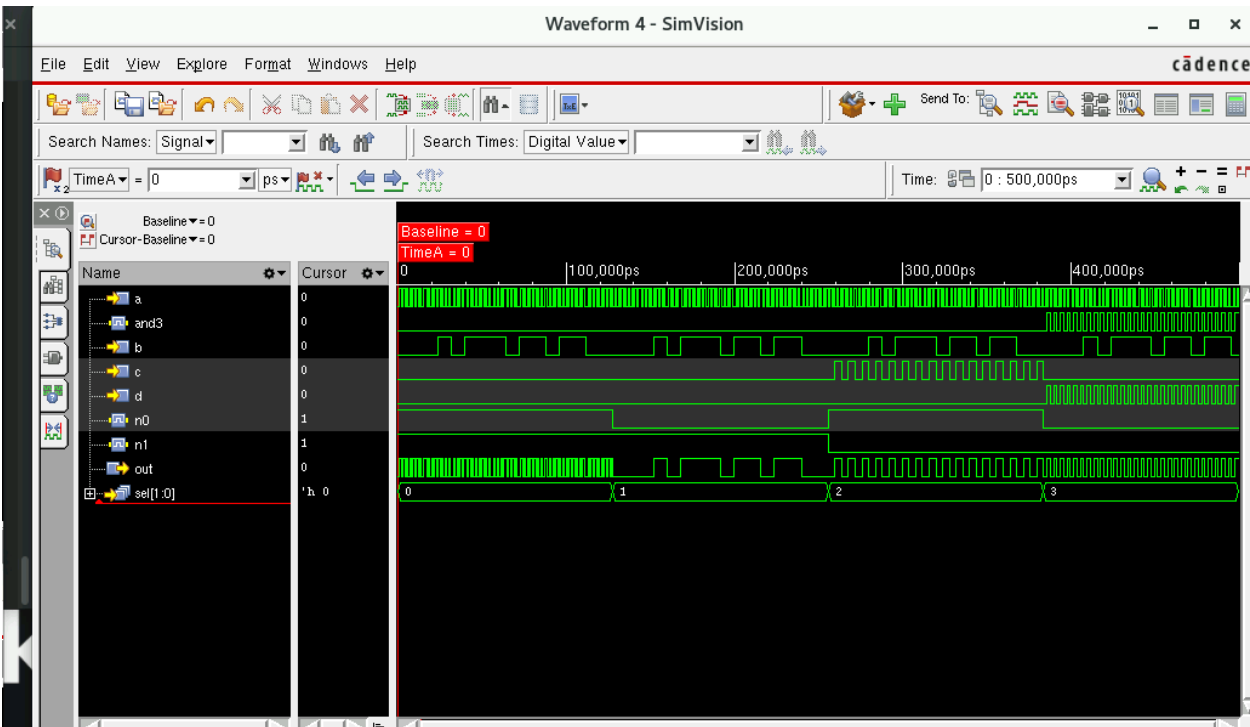

```
xcelium> # Run the simulation for 100 ns
xcelium> run 500 ns
```

Functional Verification: mux4to1							
a	b	c	d	sel	out	exp_out	Result
0	0	0	0	00	0	0	PASS
1	0	0	0	00	1	1	PASS
0	1	0	0	00	0	0	PASS
1	1	0	0	00	1	1	PASS
0	0	1	0	00	0	0	PASS
1	0	1	0	00	1	1	PASS
0	1	1	0	00	0	0	PASS
1	1	1	0	00	1	1	PASS
0	0	0	1	00	0	0	PASS
1	0	0	1	00	1	1	PASS
0	1	0	1	00	0	0	PASS
1	1	0	1	00	1	1	PASS
0	0	1	1	00	0	0	PASS
1	0	1	1	00	1	1	PASS
0	1	1	1	00	0	0	PASS
1	1	1	1	00	1	1	PASS
0	0	0	0	01	0	0	PASS
1	0	0	0	01	0	0	PASS
0	1	0	0	01	1	1	PASS
1	1	0	0	01	1	1	PASS
0	0	1	0	01	0	0	PASS
1	0	1	0	01	0	0	PASS
0	1	1	0	01	1	1	PASS
1	1	1	0	01	1	1	PASS
0	0	0	1	01	0	0	PASS
1	0	0	1	01	0	0	PASS
0	1	0	1	01	1	1	PASS
1	1	0	1	01	1	1	PASS
0	0	1	1	01	0	0	PASS
1	0	1	1	01	0	0	PASS
0	1	1	1	01	1	1	PASS
1	1	1	1	01	1	1	PASS
0	0	0	0	10	0	0	PASS
1	0	0	0	10	0	0	PASS
0	1	0	0	10	0	0	PASS
1	1	0	0	10	0	0	PASS
0	0	1	0	10	1	1	PASS
1	0	1	0	10	1	1	PASS
0	1	1	0	10	1	1	PASS
1	1	1	0	10	1	1	PASS
0	0	0	1	10	0	0	PASS

Table of MUX verification.

### Logic Unit:


The logic unit uses a 4-1 Mux as well as some basic logic gates AND OR XOR NOT. The control is based on control signals S1 S0.



A truth table below shows the signals Ai and Bi with the output Ei. I also developed a testbench with some tests which tested all possible combinations. A truth table explaining it all is below as

well as a small example of the testbench. The truth table can be extrapolated for the whole 1-bit ALU.

```
crimson:/eecs/home/aali02/EECS4612/termproject/Simulation
File Edit View Search Terminal Help
xcelium> # Run the simulation for 100 ns
xcelium> run 500 ns


=====
Functional Verification: alu_1bit
=====
Ai Bi Ap An Cin | sel | Fi Cout | Exp_Fi Exp_Cout | Result
-----
0 0 0 0 0 | 0000 | 0 0 | 0 0 | PASS
0 0 0 0 1 | 0000 | 1 0 | 1 0 | PASS
0 0 0 1 0 | 0000 | 0 0 | 0 0 | PASS
0 0 0 1 1 | 0000 | 1 0 | 1 0 | PASS
0 0 1 0 0 | 0000 | 0 0 | 0 0 | PASS
0 0 1 0 1 | 0000 | 1 0 | 1 0 | PASS
0 0 1 1 0 | 0000 | 0 0 | 0 0 | PASS
0 0 1 1 1 | 0000 | 1 0 | 1 0 | PASS
0 1 0 0 0 | 0000 | 0 0 | 0 0 | PASS
0 1 0 0 1 | 0000 | 1 0 | 1 0 | PASS
0 1 0 1 0 | 0000 | 0 0 | 0 0 | PASS
0 1 0 1 1 | 0000 | 1 0 | 1 0 | PASS
0 1 1 0 0 | 0000 | 0 0 | 0 0 | PASS
0 1 1 0 1 | 0000 | 1 0 | 1 0 | PASS
0 1 1 1 0 | 0000 | 0 0 | 0 0 | PASS
0 1 1 1 1 | 0000 | 1 0 | 1 0 | PASS
1 0 0 0 0 | 0000 | 1 0 | 1 0 | PASS
```

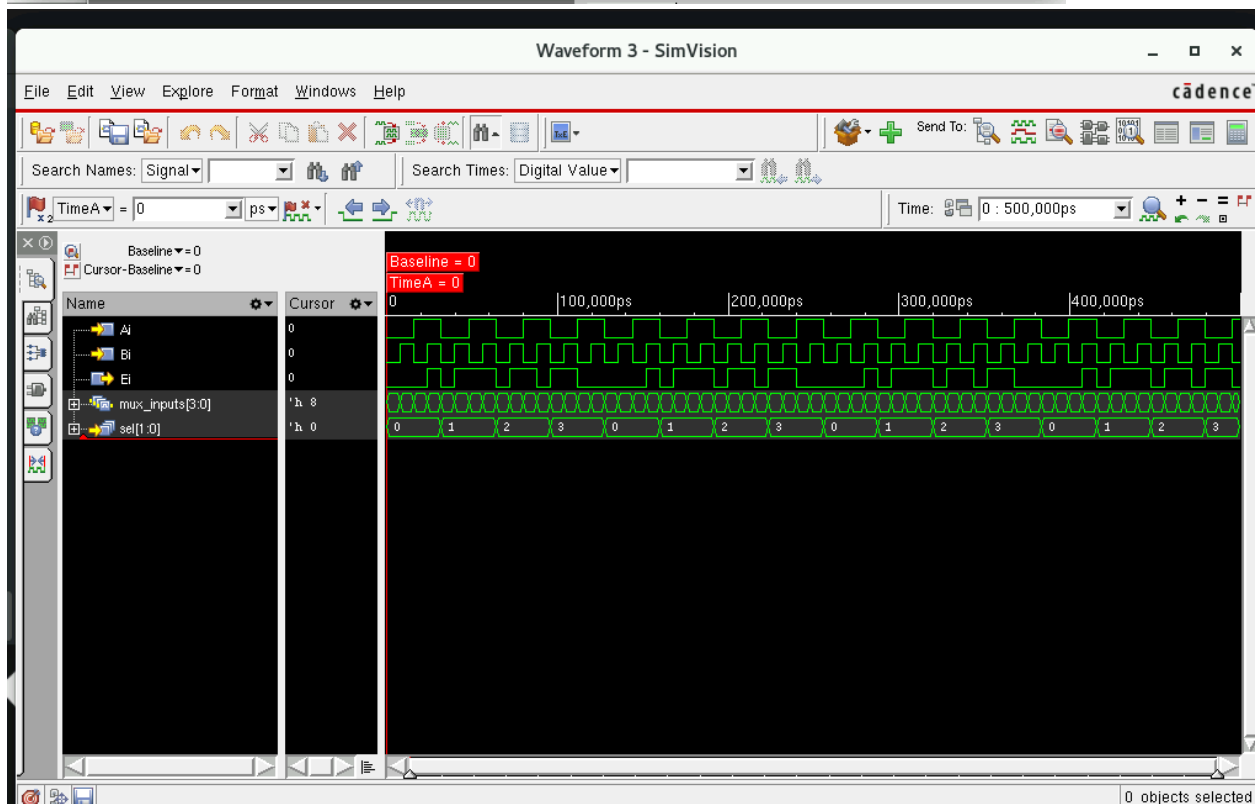

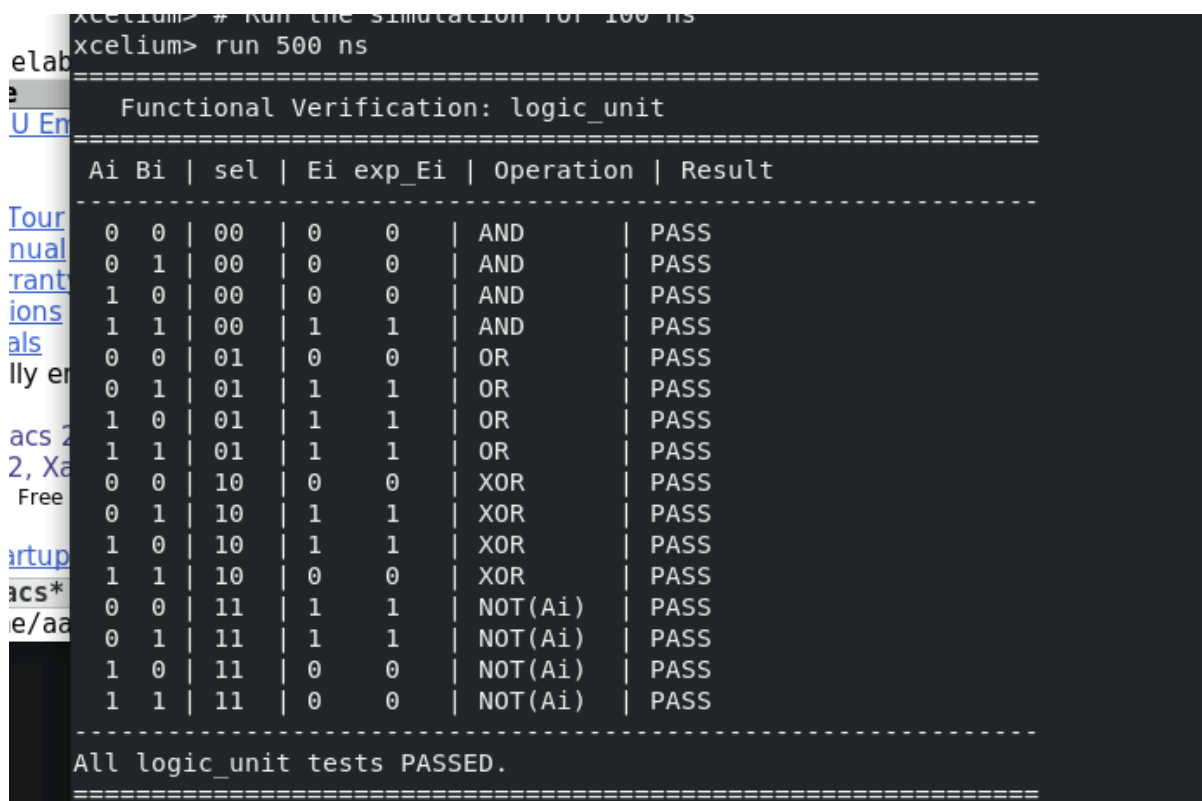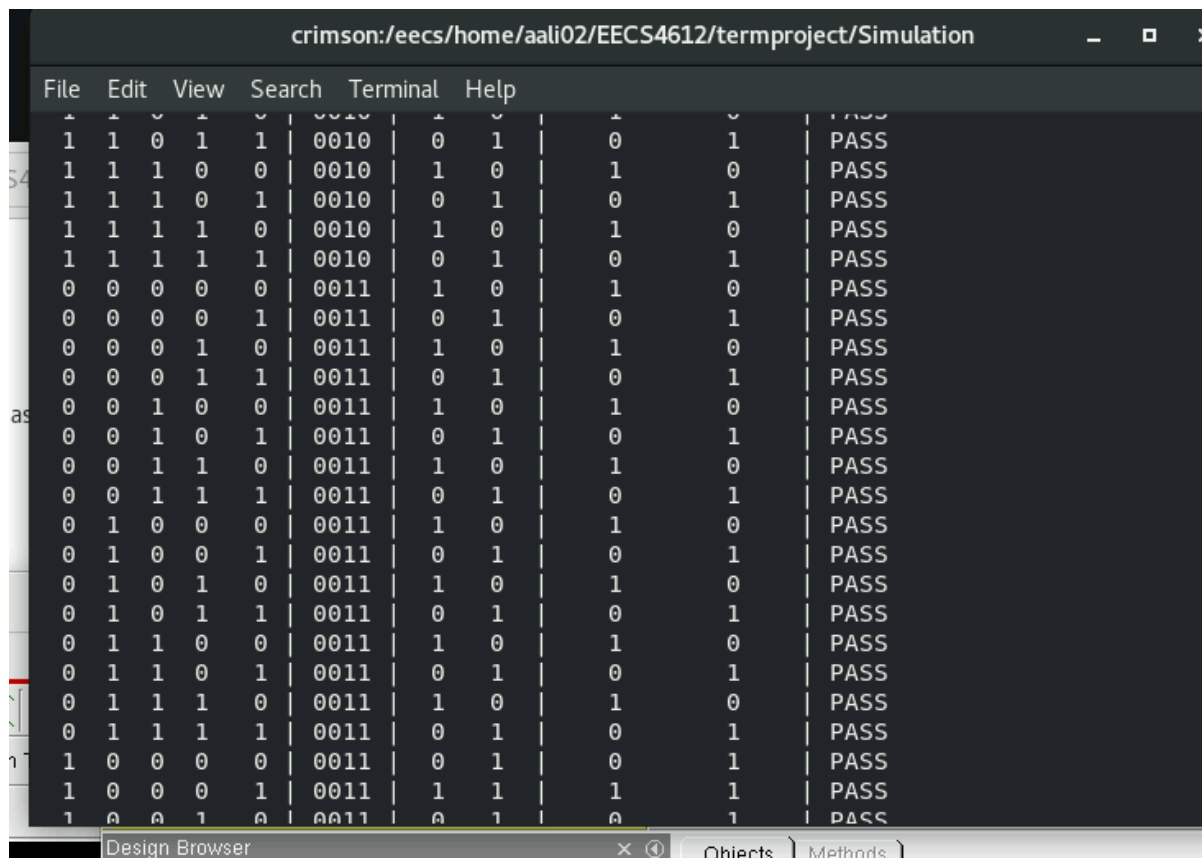



The waveform of the Logic unit is shown below. It shows the correct working according to our truth table and testbench:

### Arithmetic Unit:

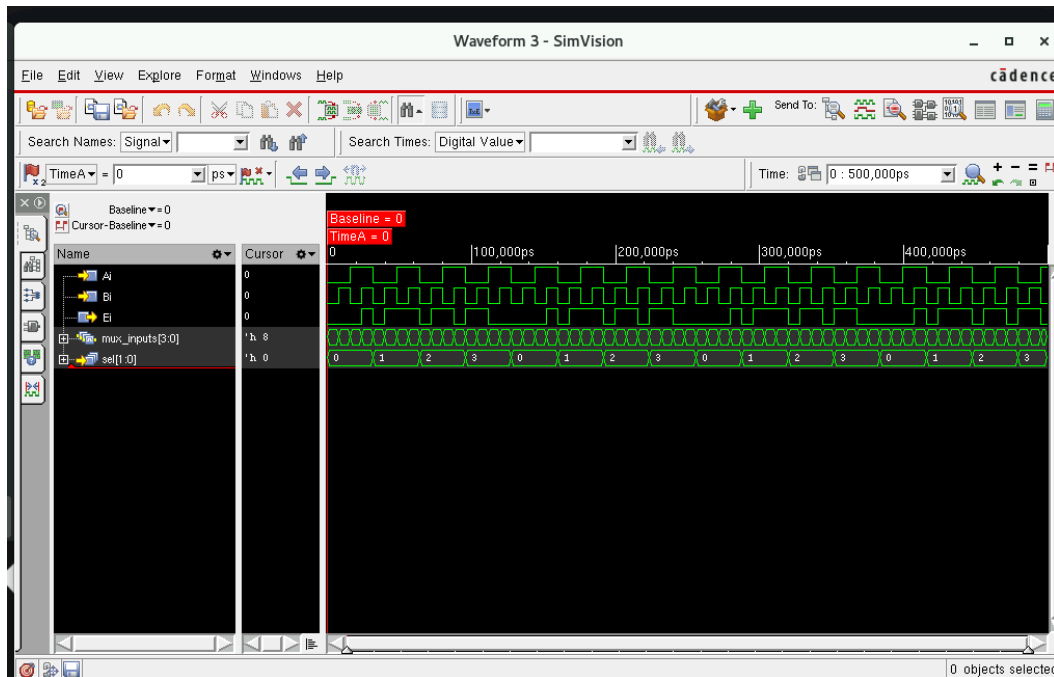

The arithmetic unit is designed to do arithmetic operations using the 4-1 mux we

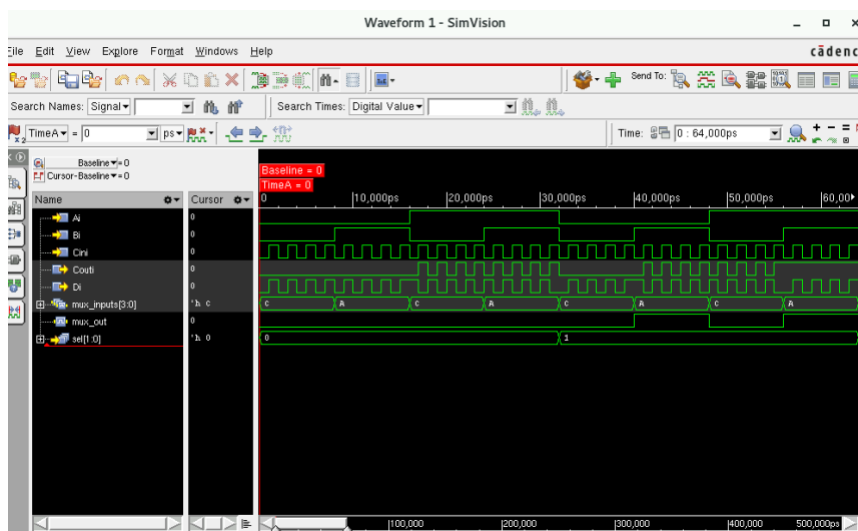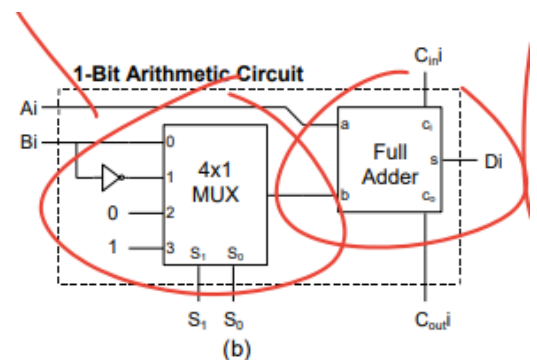designed earlier as well as a full adder which I also designed. The architecture of the arithmetic circuit is shown through this image on the right.





In the image above, we can see the simulated waveform of the Arithmetic Unit. The truth table below shows what's happening in the circuit.

S0	S1	Cin	Operation	Function
0	0	0	$F = A$	Transfer A
0	0	1	$F = A + 1$	Increment A
1	0	0	$F = A + B$	Add
1	0	1	$F = A + B + 1$	Add w/ Carry
0	1	0	$F = A \sim B$	Sub w/ borrow
0	1	1	$F = A \sim B + 1$	Subtract
1	1	0	$F = A - 1$	Decrement A
1	1	1	$F = A$	Transfer A

```
xcelium> run 500 ns
=====
Functional Verification: arithmetic_unit
=====
Ai Bi Cin | sel | Di Cout | Exp_Di Exp_Cout | Operation | Result
-----
0 0 0 | 00 | 0 0 | 0 0 | Ai + 0 + Cini | PASS
0 0 1 | 00 | 1 0 | 1 0 | Ai + 0 + Cini | PASS
0 1 0 | 00 | 0 0 | 0 0 | Ai + 0 + Cini | PASS
0 1 1 | 00 | 1 0 | 1 0 | Ai + 0 + Cini | PASS
1 0 0 | 00 | 1 0 | 1 0 | Ai + 0 + Cini | PASS
1 0 1 | 00 | 0 1 | 0 1 | Ai + 0 + Cini | PASS
1 1 0 | 00 | 1 0 | 1 0 | Ai + 0 + Cini | PASS
1 1 1 | 00 | 0 1 | 0 1 | Ai + 0 + Cini | PASS
0 0 0 | 01 | 0 0 | 0 0 | Ai + Bi + Cini | PASS
0 0 1 | 01 | 1 0 | 1 0 | Ai + Bi + Cini | PASS
0 1 0 | 01 | 1 0 | 1 0 | Ai + Bi + Cini | PASS
0 1 1 | 01 | 0 1 | 0 1 | Ai + Bi + Cini | PASS
1 0 0 | 01 | 1 0 | 1 0 | Ai + Bi + Cini | PASS
1 0 1 | 01 | 0 1 | 0 1 | Ai + Bi + Cini | PASS
1 1 0 | 01 | 0 1 | 0 1 | Ai + Bi + Cini | PASS
1 1 1 | 01 | 1 1 | 1 1 | Ai + Bi + Cini | PASS
0 0 0 | 10 | 1 0 | 1 0 | Ai + ~Bi + Cini | PASS
0 0 1 | 10 | 0 1 | 0 1 | Ai + ~Bi + Cini | PASS
0 1 0 | 10 | 0 0 | 0 0 | Ai + ~Bi + Cini | PASS
0 1 1 | 10 | 1 0 | 1 0 | Ai + ~Bi + Cini | PASS
1 0 0 | 10 | 0 1 | 0 1 | Ai + ~Bi + Cini | PASS
1 0 1 | 10 | 1 1 | 1 1 | Ai + ~Bi + Cini | PASS
1 1 0 | 10 | 1 0 | 1 0 | Ai + ~Bi + Cini | PASS
1 1 1 | 10 | 0 1 | 0 1 | Ai + ~Bi + Cini | PASS
0 0 0 | 11 | 1 0 | 1 0 | Ai + 1 + Cini | PASS
0 0 1 | 11 | 0 1 | 0 1 | Ai + 1 + Cini | PASS
0 1 0 | 11 | 1 0 | 1 0 | Ai + 1 + Cini | PASS
0 1 1 | 11 | 0 1 | 0 1 | Ai + 1 + Cini | PASS
1 0 0 | 11 | 0 1 | 0 1 | Ai + 1 + Cini | PASS
1 0 1 | 11 | 1 1 | 1 1 | Ai + 1 + Cini | PASS
1 1 0 | 11 | 0 1 | 0 1 | Ai + 1 + Cini | PASS
1 1 1 | 11 | 1 1 | 1 1 | Ai + 1 + Cini | PASS
-----
All arithmetic_unit tests PASSED.
```

Now that all the units have been individually simulated and verified, lets move on to the resulting area and power.

### Area and Power of 1-bit ALU:

#### Power Report:

genus_alu_1bit_power.rep ~/EECS4612/tempproject/Synthesis/reports					
Instance: /alu_1bit Power Unit: W PDB Frames: /stim#0/frame#0					
Category	Leakage	Internal	Switching	Total	Row%
memory	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
register	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
latch	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
logic	2.11523e-09	1.68016e-08	1.18341e-06	1.20232e-06	100.00%
bbox	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
clock	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
pad	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
pm	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
Subtotal	2.11523e-09	1.68016e-08	1.18341e-06	1.20232e-06	100.00%
Percentage	0.18%	1.40%	98.43%	100.00%	100.00%


This is the power report of the ALU. We can see the total power consumed is  $1.202 \times 10^{-6}$  W and switching takes up around 98% of the power. Very low leakage power as well showing efficiency.

#### Area Report:

genus_alu_1bit_area.rep ~/EECS4612/tempproject/Synthesis/reports			
Generated by: Genus(TM) Synthesis Solution 21.17-s066_1 Generated on: Dec 12 2025 07:25:02 pm Module: alu_1bit Operating conditions: PVT 009V 125C (balanced_tree) Wireload mode: enclosed Area mode: timing library			
Gate	Instances	Area	Library
ADDFHXL	1	7.524	slow_vdd1v0
AND2XL	1	1.368	slow_vdd1v0
AND3XL	1	2.052	slow_vdd1v0
CLKBUF2X0	2	16.416	slow_vdd1v0
CLKMX2X12	1	6.498	slow_vdd1v0
INVXL	1	0.684	slow_vdd1v0
MX2X1	1	2.394	slow_vdd1v0
MX2XL	2	4.788	slow_vdd1v0
MX4XL	1	7.182	slow_vdd1v0
NAND2X1	1	1.026	slow_vdd1v0
NOR2BX1	1	1.368	slow_vdd1v0
NOR2X1	1	1.026	slow_vdd1v0
OR2XL	1	1.368	slow_vdd1v0
total	15	53.694	
Type	Instances	Area	Area %
inverter	1	0.684	1.3
buffer	2	16.416	30.6
logic	12	36.594	68.2
physical_cells	0	0.000	0.0
total	15	53.694	100.0



The total area of the 1-bit ALU is  $53.694 \times 10^{-6}$  meters squared. Other details pertaining to the area are also shown in the diagram.

## Gate Level Netlist Schematic:

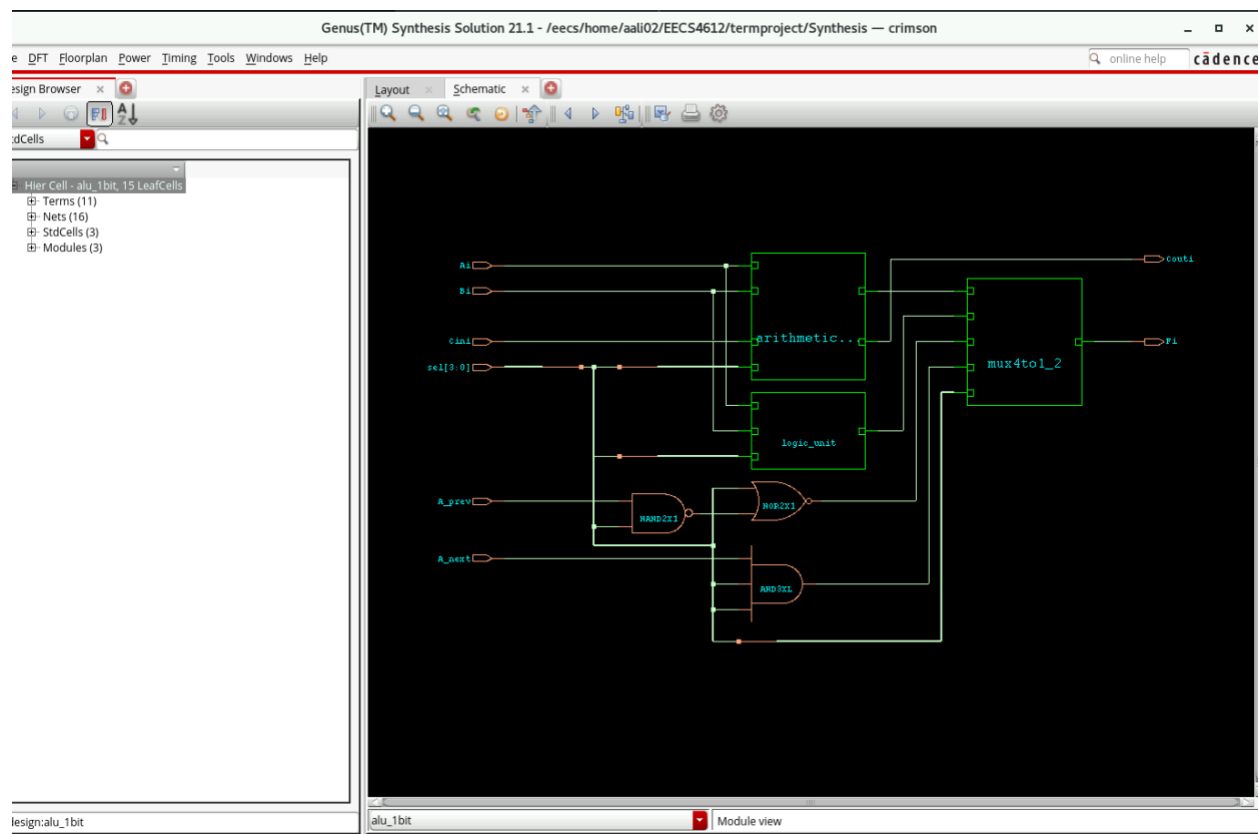


The figure above shows the schematic of the synthesized 1-bit ALU. It has all the functional units that we created before.

## Physical Design of 1-bit ALU

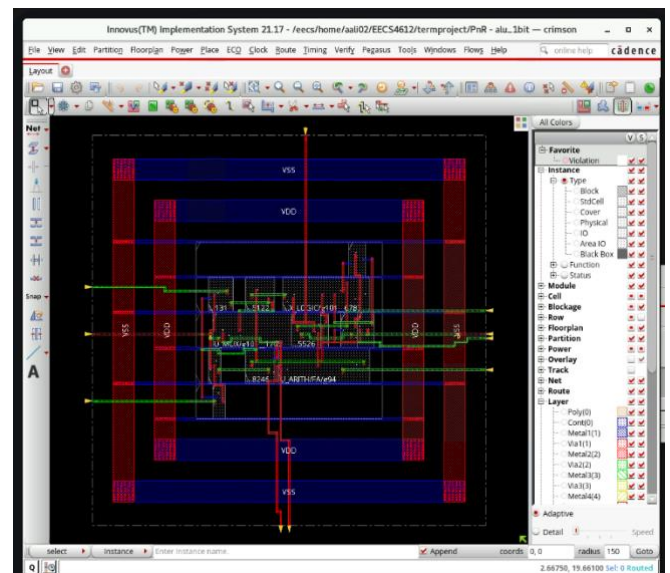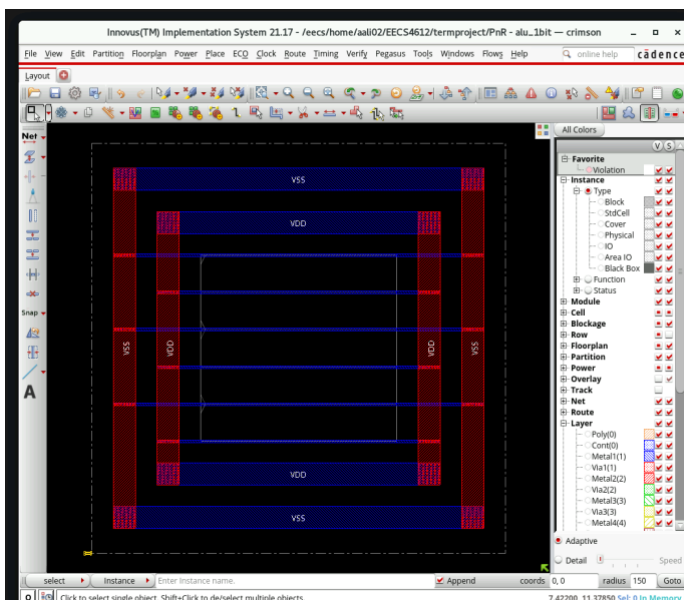

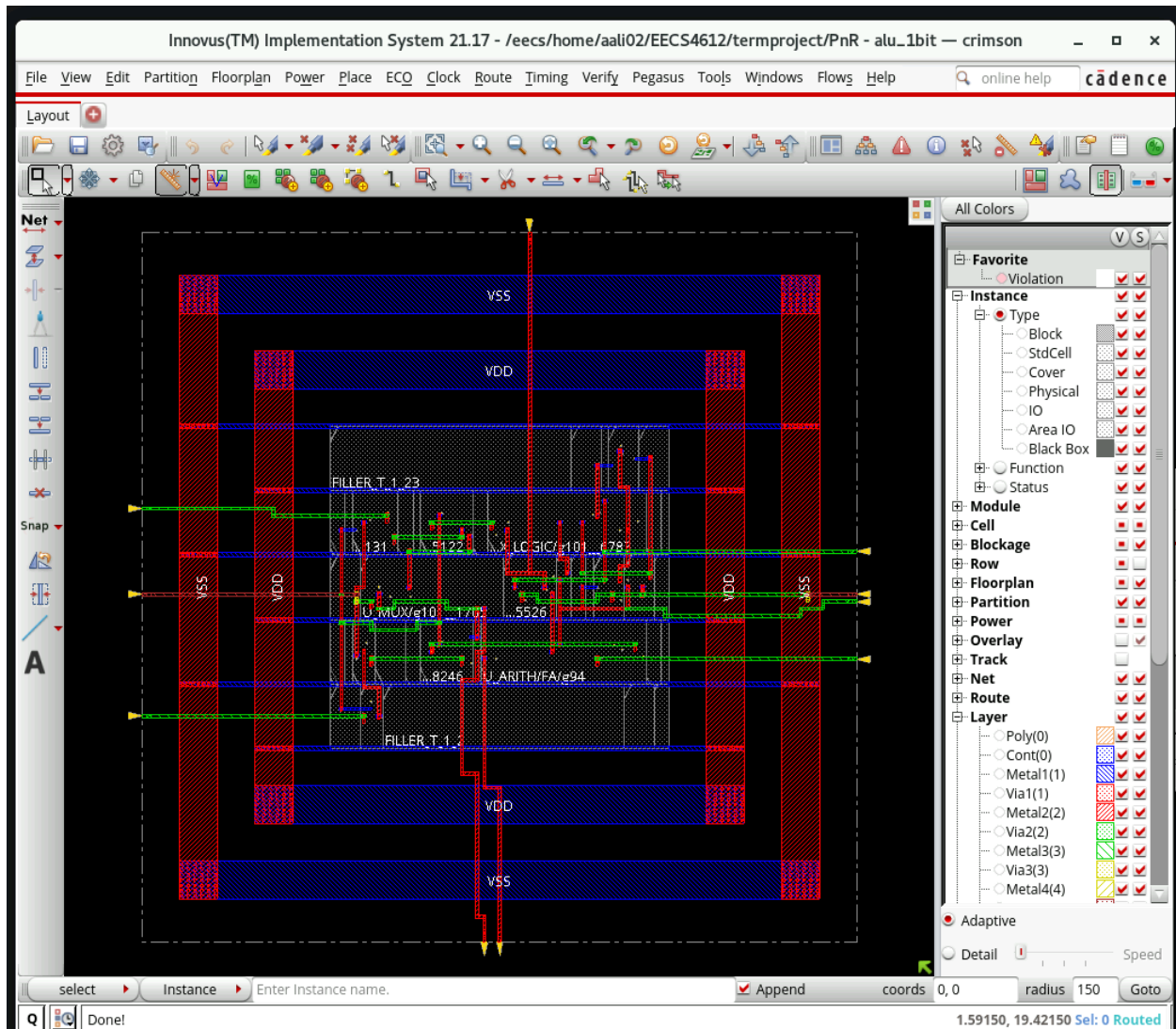The above screenshots show the power routing and standard cell placement. The screenshot below shows the final routing with filler.



## DRC and Connectivity Verification

```
crimson:/eecs/home/aali02/EECS4612/termproject/PnR
File Edit View Search Terminal Help
#Total number of fails = 0
#Complete globalDetailRoute on Fri Dec 12 19:55:56 2025
#
#Default setup view is reset to worst_case.
#Default setup view is reset to worst_case.
AAE_INFO: Post Route call back at the end of routeDesign
#routeDesign: cpu time = 00:00:01, elapsed time = 00:00:01, memory = 1935.34 (MB), peak = 1963.80 (MB)

*** Summary of all messages that are not suppressed in this session:
Severity ID Count Summary
WARNING NRDB-2005 4 %s %s has special wires but no definitio...
WARNING NRIG-1303 2 The congestion map does not match the GC...
WARNING NRIF-90 1 Option setNanoRouteMode -routeBottomRout...
WARNING NRIF-91 1 Option setNanoRouteMode -routeTopRouting...
*** Message Summary: 5 warning(s), 0 error(s)

innovus l> **WARN: (IMPSP-5217): addFiller command is running on a postRoute database. It is recommended to be f
ollowed by ecoRoute -target command to make the DRC clean.
Type 'man IMPSP-5217' for more detail.
*INFO: Adding fillers to top-module.
*INFO: Added 0 filler inst (cell FILL64 / prefix FILLER).
*INFO: Added 2 filler insts (cell FILL32 / prefix FILLER).
*INFO: Added 0 filler inst (cell FILL16 / prefix FILLER).
*INFO: Added 0 filler inst (cell FILL8 / prefix FILLER).
*INFO: Added 6 filler insts (cell FILL4 / prefix FILLER).
*INFO: Added 10 filler insts (cell FILL2 / prefix FILLER).
*INFO: Added 8 filler insts (cell FILL1 / prefix FILLER).
*INFO: Total 26 filler insts added - prefix FILLER (CPU: 0:00:00.0).
For 26 new insts, innovus l> #-check_ndr_spacing auto # enums={true false auto}, default=auto, user se
tting
#-check_same_via_cell true # bool, default=false, user setting
#-exclude_pg_net true # bool, default=false, user setting
#-report_alu_lbit.drc.rpt # string, default="", user setting
*** Starting Verify DRC (MEM: 2670.7) ***

VERIFY DRC ..... Starting Verification
VERIFY DRC ..... Initializing
VERIFY DRC ..... Deleting Existing Violations
VERIFY DRC ..... Creating Sub-Areas
VERIFY DRC ..... Using new threading
VERIFY DRC ..... Sub-Area: {0.0000 0.0000 19.0000 18.8100} 1 of 1
VERIFY DRC ..... Sub-Area : 1 complete 0 Viols.

Verification Complete : 0 Viols.

*** End Verify DRC (CPU: 0:00:00.0 ELAPSED TIME: 0.00 MEM: 256.1M) ***

innovus l>

Verification Complete : 0 Viols.

*** End Verify DRC (CPU: 0:00:00.0 ELAPSED TIME: 0.00 MEM: 256.1M) ***

innovus l> VERIFY_CONNECTIVITY use new engine.

***** Start: VERIFY CONNECTIVITY *****
Start Time: Fri Dec 12 19:58:12 2025

Design Name: alu_lbit
Database Units: 2000
Design Boundary: (0.0000, 0.0000) (19.0000, 18.8100)
Error Limit = 1000; Warning Limit = 50
Check all nets

Begin Summary
Found no problems or warnings.
End Summary


End Time: Fri Dec 12 19:58:12 2025
Time Elapsed: 0:00:00.0

***** End: VERIFY CONNECTIVITY *****
Verification Complete : 0 Viols. 0 Wrngs.
(CPU Time: 0:00:00.0 MEM: 0.000M)

innovus l>
```
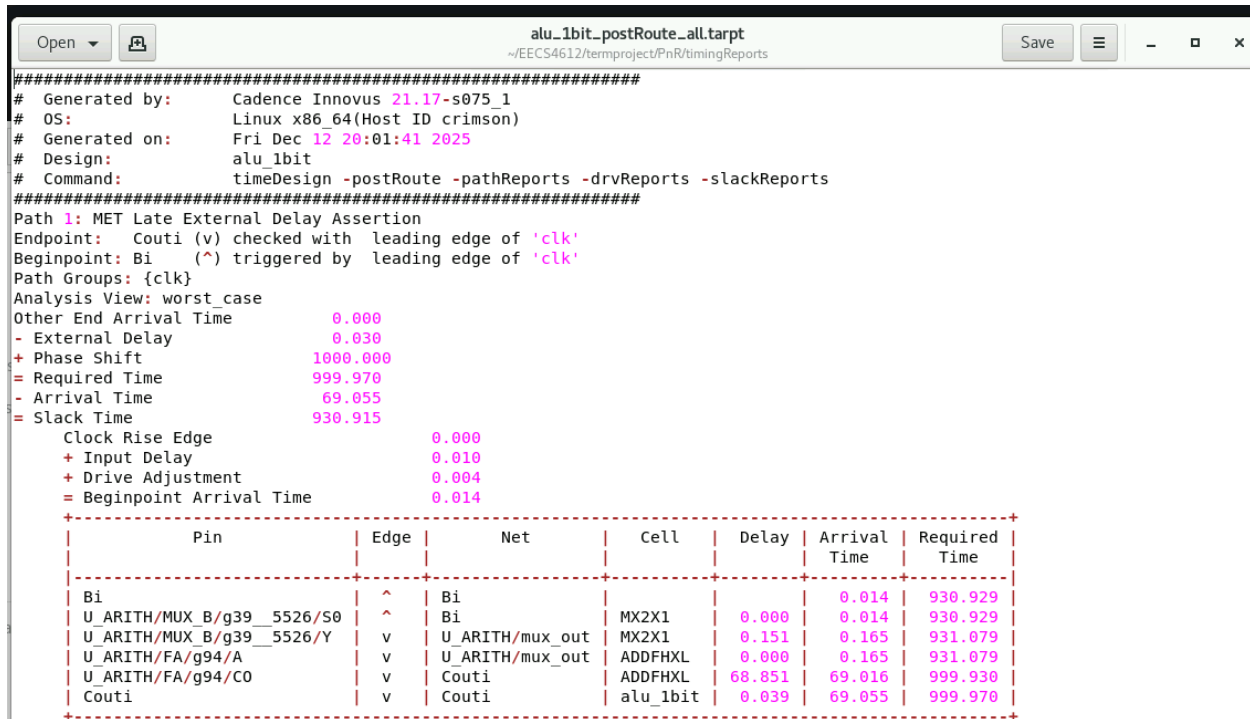
## Estimating Speed using Timing Analysis:

Since we cannot do clock tree synthesis because there is no clock, I used timing analysis.



```
#####
# Generated by: Cadence Innovus 21.17-s075_1
# OS: Linux x86_64(Host ID crimson)
# Generated on: Fri Dec 12 20:01:41 2025
# Design: alu_1bit
# Command: timeDesign -postRoute -pathReports -drvReports -slackReports
#####
Path 1: MET Late External Delay Assertion
Endpoint: Couti (v) checked with leading edge of 'clk'
Beginpoint: Bi (^) triggered by leading edge of 'clk'
Path Groups: {clk}
Analysis View: worst_case
Other End Arrival Time 0.000
- External Delay 0.030
+ Phase Shift 1000.000
= Required Time 999.970
- Arrival Time 69.055
= Slack Time 930.915
Clock Rise Edge 0.000
+ Input Delay 0.010
+ Drive Adjustment 0.004
= Beginpoint Arrival Time 0.014
+-----+-----+-----+-----+-----+-----+
| Pin | Edge | Net | Cell | Delay | Arrival Time | Required Time |
+-----+-----+-----+-----+-----+-----+
| Bi | ^ | Bi | | | 0.014 | 930.929 |
| U_ARITH/MUX_B/g39_5526/S0 | ^ | Bi | MX2X1 | 0.000 | 0.014 | 930.929 |
| U_ARITH/MUX_B/g39_5526/Y | v | U_ARITH/mux_out | MX2X1 | 0.151 | 0.165 | 931.079 |
| U_ARITH/FA/g94/A | v | U_ARITH/mux_out | ADDFHXL | 0.000 | 0.165 | 931.079 |
| U_ARITH/FA/g94/C0 | v | Couti | ADDFHXL | 68.851 | 69.016 | 999.930 |
| Couti | v | Couti | alu_1bit | 0.039 | 69.055 | 999.970 |
+-----+-----+-----+-----+-----+-----+

```

**Estimate Max Speed:** we have the arrival time so we need to simply do  $f_{max} = 1 / \text{critical path delay}$


$$f_{max} = \frac{1}{69.055 \times 10^{-9}} = 14.48 \text{ mhz}$$

So, the total max speed the circuit can operate under is 14.48 mhz.

# Part 2: 32-Bit ALUS
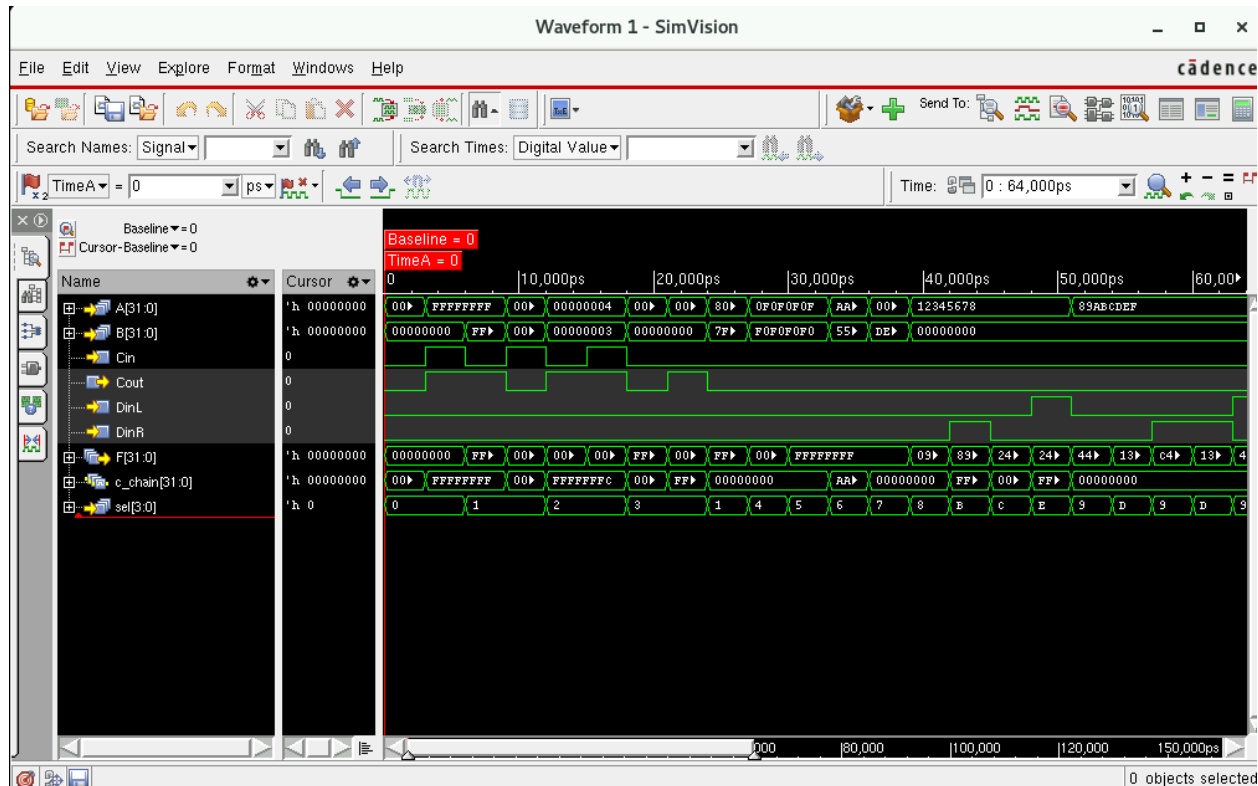
## Modular 32-Bit ALU:

The format is as follows: information about the modular ALU followed by information about the behavioral ALU.



The above screenshot shows the waveform for the modular ALU (1-bit instantiated 32 times). We can see that everything works in the waveform. Below is a couple screenshots of the testbench verification.

```
=====
Functional Verification: 32-bit Modular ALU (self-check)
=====

---- Arithmetic tests ----

ARITH: Transfer A | sel=0x0 A=0x00000000 B=0x00000000 Cin=0 DinL=0 DinR=0
Expected: F=0x00000000 Cout=0 | Got: F=0x00000000 Cout=0
[PASS] Arithmetic
-----

ARITH: Increment A (Cin=1) | sel=0x0 A=0xffffffff B=0x00000000 Cin=1 DinL=0 DinR=0
Expected: F=0x00000000 Cout=1 | Got: F=0x00000000 Cout=1
[PASS] Arithmetic
-----

ARITH: A + B (max) | sel=0x1 A=0xffffffff B=0xffffffff Cin=0 DinL=0 DinR=0
Expected: F=0xfffffffffe Cout=1 | Got: F=0xfffffffffe Cout=1
[PASS] Arithmetic
-----

ARITH: A + B + 1 | sel=0x1 A=0x00000001 B=0x00000001 Cin=1 DinL=0 DinR=0
Expected: F=0x00000003 Cout=0 | Got: F=0x00000003 Cout=0
[PASS] Arithmetic
-----

ARITH: A - B - 1 (Cin=0) | sel=0x2 A=0x00000004 B=0x00000003 Cin=0 DinL=0 DinR=0
Expected: F=0x00000000 Cout=1 | Got: F=0x00000000 Cout=1
[PASS] Arithmetic
-----

ARITH: A - B (Cin=1) | sel=0x2 A=0x00000004 B=0x00000003 Cin=1 DinL=0 DinR=0
Expected: F=0x00000001 Cout=1 | Got: F=0x00000001 Cout=1
[PASS] Arithmetic
-----
```

```
Chimera/EECS/home/adam2/EECS-662/termproject/simulation

File Edit View Search Terminal Help

-----

LOGIC: NOT A | sel=0x7 A=0x00000000 B=0xdeadbeef Cin=0 DinL=0 DinR=0
Expected: F=0xfffffffff Cout=0 | Got: F=0xfffffffff Cout=0
[PASS] Logic/Shift
-----

---- Shift tests ----

SHIFT: Right (DR=0) | sel=0x8 A=0x12345678 B=0x00000000 Cin=0 DinL=0 DinR=0
Expected: F=0x091a2b3c Cout=0 | Got: F=0x091a2b3c Cout=0
[PASS] Logic/Shift
-----

SHIFT: Right (DR=1, sel varied) | sel=0xb A=0x12345678 B=0x00000000 Cin=0 DinL=0 DinR=1
Expected: F=0x891a2b3c Cout=0 | Got: F=0x891a2b3c Cout=0
[PASS] Logic/Shift
-----

SHIFT: Left (DL=0) | sel=0xc A=0x12345678 B=0x00000000 Cin=0 DinL=0 DinR=0
Expected: F=0x2468acf0 Cout=0 | Got: F=0x2468acf0 Cout=0
[PASS] Logic/Shift
-----

SHIFT: Left (DL=1, sel varied) | sel=0xe A=0x12345678 B=0x00000000 Cin=0 DinL=1 DinR=0
Expected: F=0x2468acf1 Cout=0 | Got: F=0x2468acf1 Cout=0
[PASS] Logic/Shift
-----

SHIFT SWEEP: Right | sel=0x9 A=0x89abcdef B=0x00000000 Cin=0 DinL=0 DinR=0
Expected: F=0x44d5e6f7 Cout=0 | Got: F=0x44d5e6f7 Cout=0
[PASS] Logic/Shift
-----
```



```
crimson:/eecs/home/aali02/EECS4612/termproject/Simulation

File Edit View Search Terminal Help

-----

RANDOM | sel=0xa A=0xafd8565f B=0x22290d44 Cin=1 DinL=1 DinR=0
Expected: F=0x57ec2b2f Cout=0 | Got: F=0x57ec2b2f Cout=0
[PASS] Logic/Shift
-----

RANDOM | sel=0xf A=0x14cfc129 B=0xf682e2ed Cin=0 DinL=1 DinR=1
Expected: F=0x299f8253 Cout=0 | Got: F=0x299f8253 Cout=0
[PASS] Logic/Shift
-----

RANDOM | sel=0xe A=0x3cf11979 B=0x2231ff44 Cin=0 DinL=0 DinR=1
Expected: F=0x79e232f2 Cout=0 | Got: F=0x79e232f2 Cout=0
[PASS] Logic/Shift
-----

RANDOM | sel=0xe A=0x6e5daddc B=0xcd5ebc9a Cin=1 DinL=1 DinR=0
Expected: F=0xdcbb5bb9 Cout=0 | Got: F=0xdcbb5bb9 Cout=0
[PASS] Logic/Shift
-----


RANDOM | sel=0x8 A=0xb3d97667 B=0x8531340a Cin=0 DinL=0 DinR=1
Expected: F=0xd9ecbb33 Cout=0 | Got: F=0xd9ecbb33 Cout=0
[PASS] Logic/Shift
-----

RANDOM | sel=0xd A=0x4a74bf94 B=0x49c65d93 Cin=0 DinL=1 DinR=1
Expected: F=0x94e97f29 Cout=0 | Got: F=0x94e97f29 Cout=0
[PASS] Logic/Shift
-----

All functional verification tests completed.
```

There are quite a few tests, so I did not have space to put them all, but they pass. You can also run the testbench for yourself to verify.

## Behavioral 32-bit ALU:

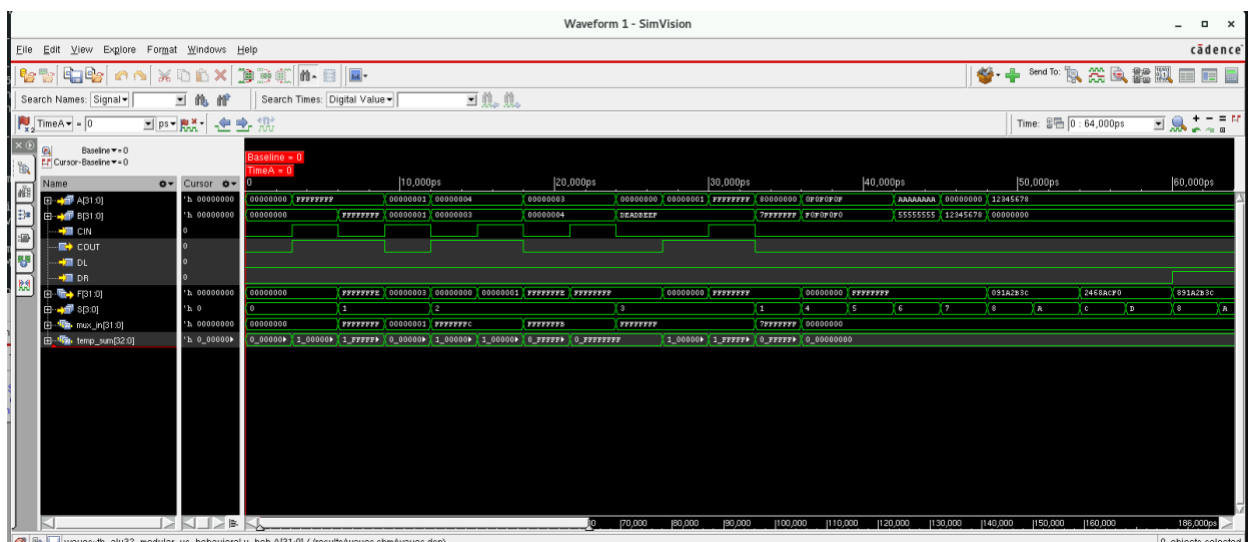

```
crimson:/eecs/home/aali02/EECS4612/termproject/Simulation

File Edit View Search Terminal Help

Self-checking TB: alu_32bit_behavioral (32-bit)

---- Arithmetic tests ----

ARITH: Transfer A (Cin=0) | S=0x0 A=0x00000000 B=0x00000000 CIN=0 DL=0 DR=0
Expected: F=0x00000000 COUT=0 | Got: F=0x00000000 COUT=0
[PASS]

ARITH: A + 0 + Cin (increment edge) | S=0x0 A=0xffffffff B=0x00000000 CIN=1 DL=0 DR=0
Expected: F=0x00000000 COUT=1 | Got: F=0x00000000 COUT=1
[PASS]

ARITH: A + B (max + max) | S=0x1 A=0xffffffff B=0xffffffff CIN=0 DL=0 DR=0
Expected: F=0xffffffff COUT=1 | Got: F=0xffffffff COUT=1
[PASS]

ARITH: A + B + Cin | S=0x1 A=0x00000001 B=0x00000001 CIN=1 DL=0 DR=0
Expected: F=0x00000003 COUT=0 | Got: F=0x00000003 COUT=0
[PASS]

ARITH: A + ~B + Cin (A-B-1) | S=0x2 A=0x00000004 B=0x00000003 CIN=0 DL=0 DR=0
Expected: F=0x00000000 COUT=1 | Got: F=0x00000000 COUT=1
[PASS]

ARITH: A + ~B + Cin (A-B) | S=0x2 A=0x00000004 B=0x00000003 CIN=1 DL=0 DR=0
Expected: F=0x00000001 COUT=1 | Got: F=0x00000001 COUT=1
[PASS]

ARITH: A + 0xFFFF.FFFF + 0 (decrement underflow) | S=0x3 A=0x00000000 B=0x00000000 CIN=0 DL=0 DR=0
Expected: F=0xffffffff COUT=0 | Got: F=0xffffffff COUT=0
[PASS]
```

```
Downloads tb_alu_32bit_behavioral crimson:/eecs/home/aali02/EECS4612/termproject/Simulation

File Edit View Search Terminal Help

SHIFT: left, DL=0 | S=0xc A=0x12345678 B=0x00000000 CIN=0 DL=0 DR=0
Expected: F=0x2468acf0 COUT=0 | Got: F=0x2468acf0 COUT=0
[PASS]

SHIFT: left, DL=1 | S=0xc A=0x12345678 B=0x00000000 CIN=0 DL=1 DR=0
Expected: F=0x2468acf1 COUT=0 | Got: F=0x2468acf1 COUT=0
[PASS]

---- Randomized sweep ----

RANDOM | S=0xd A=0x12153524 B=0xc0895e81 CIN=1 DL=1 DR=1
Expected: F=0x242a6a49 COUT=0 | Got: F=0x242a6a49 COUT=0
[PASS]

RANDOM | S=0xd A=0xb2c28465 B=0x89375212 CIN=1 DL=1 DR=0
Expected: F=0x658508cb COUT=0 | Got: F=0x658508cb COUT=0
[PASS]

RANDOM | S=0xa A=0x76d457ed B=0x462df78c CIN=1 DL=0 DR=1
Expected: F=0xbb6a2bf6 COUT=0 | Got: F=0xbb6a2bf6 COUT=0
[PASS]

RANDOM | S=0xe A=0x72aff7e5 B=0xbbd27277 CIN=0 DL=1 DR=0
Expected: F=0xe55fefcb COUT=0 | Got: F=0xe55fefcb COUT=0
[PASS]

RANDOM | S=0x5 A=0xf4007ae8 B=0xe2ca4ec5 CIN=0 DL=1 DR=1
Expected: F=0xf6ca7eed COUT=0 | Got: F=0xf6ca7eed COUT=0
[PASS]

RANDOM | S=0xd A=0xb1ef6263 B=0x0573870a CIN=0 DL=0 DR=0
```

```

[PASS]
-----

RANDOM | S=0x9  A=0x0fd28f1f  B=0xe9ebf6d3  CIN=1  DL=0  DR=1
Expected: F=0x87e9478f  COUT=0 | Got: F=0x87e9478f  COUT=0
[PASS]
-----

RANDOM | S=0xc  A=0x9ff2ae3f  B=0x150caf2a  CIN=0  DL=0  DR=0
Expected: F=0x3fe55c7e  COUT=0 | Got: F=0x3fe55c7e  COUT=0
[PASS]
-----

RANDOM | S=0x3  A=0x7d3599fa  B=0x937dbc26  CIN=1  DL=1  DR=1
Expected: F=0x7d3599fa  COUT=1 | Got: F=0x7d3599fa  COUT=1
[PASS]
-----


RANDOM | S=0xa  A=0xafd8565f  B=0x22290d44  CIN=1  DL=1  DR=0
Expected: F=0x57ec2b2f  COUT=0 | Got: F=0x57ec2b2f  COUT=0
[PASS]
-----


All checks complete.

```

In the above screenshots we can see the simulation and verification of the 32 Bit Behavioral ALU. This is the one that we are going to use because of the improvements in area and power which we will analyze later in the report. The 32 bit behavioral ALU is a lot better in all metrics compared to the 32 bit modular ALU.

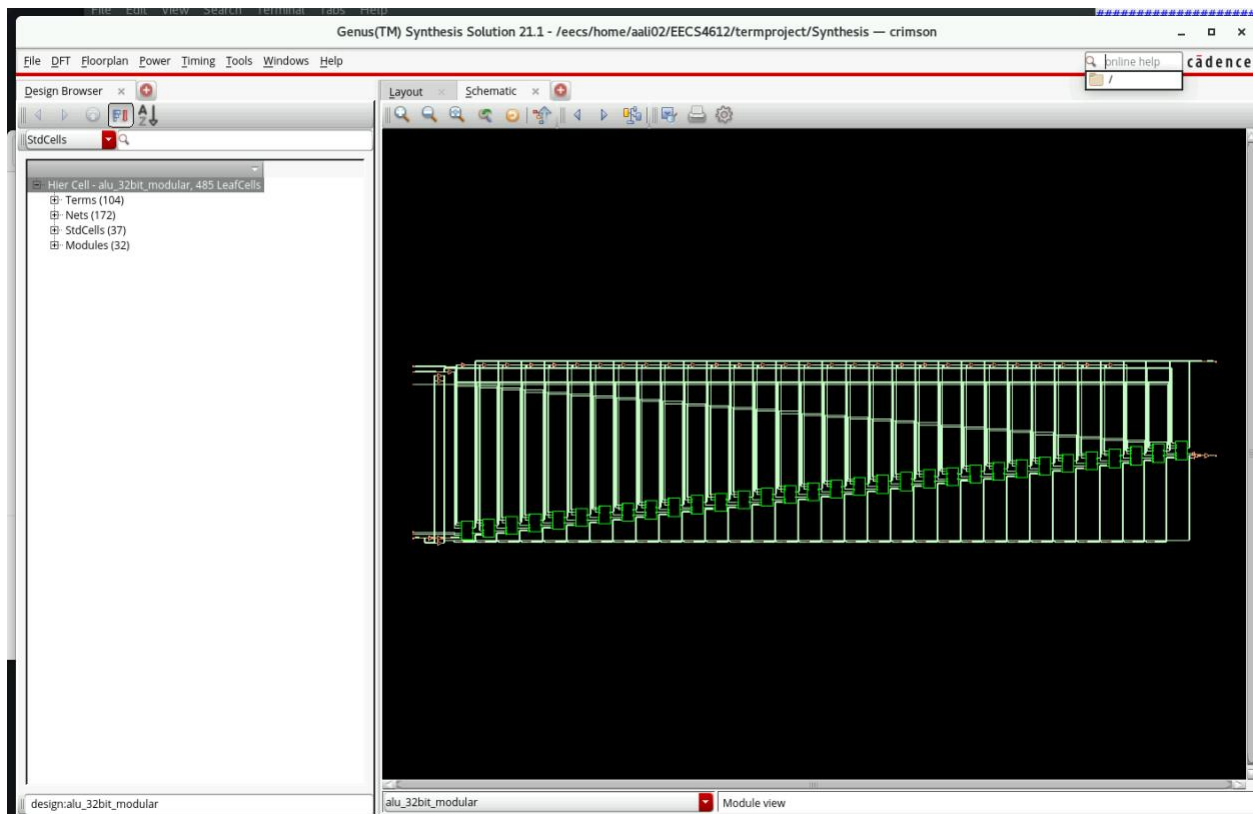
### Gate level schematic of Modular and Behavioral 32-bit ALU:



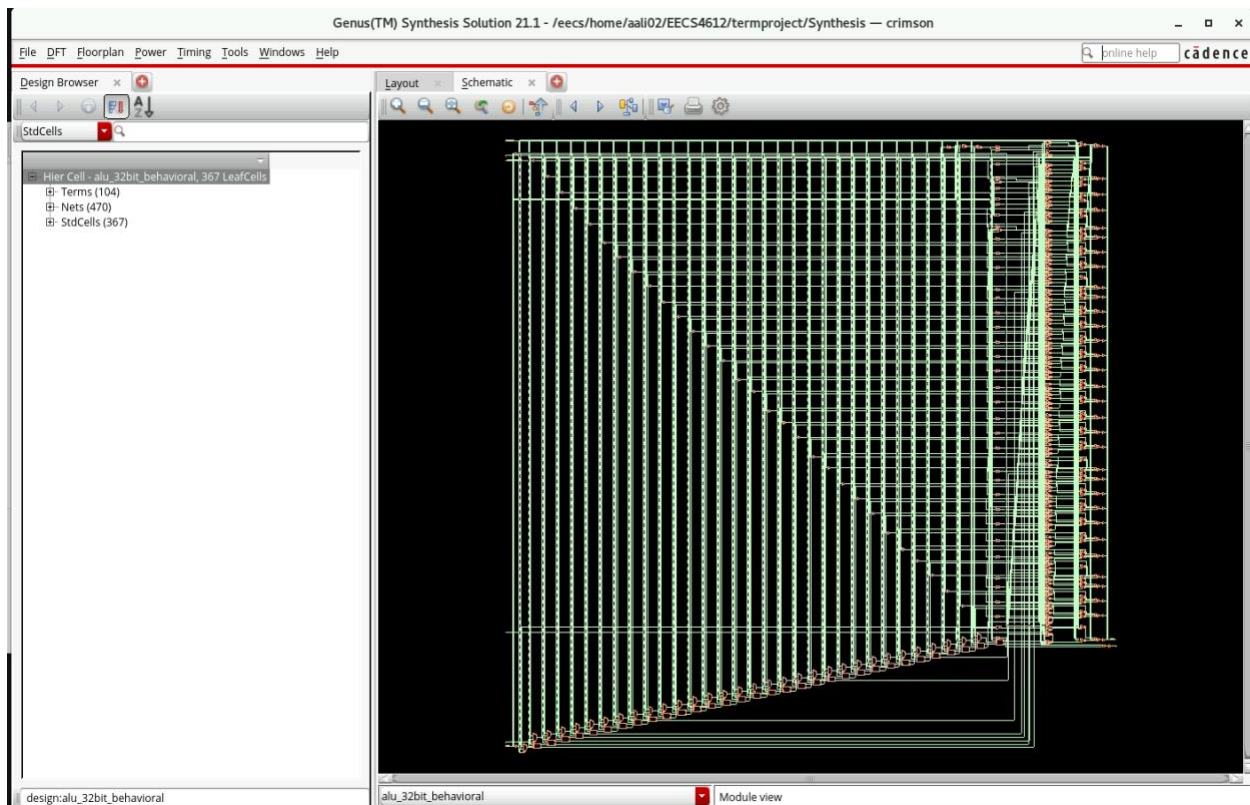


At this stage, both designs have been verified and we have checked to make sure that each component is working properly. We can now move forward
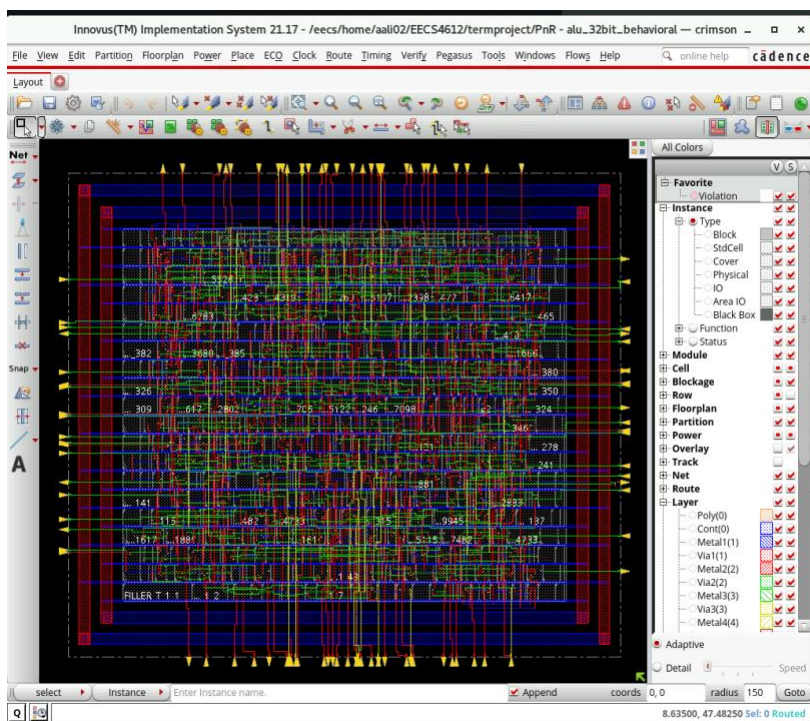
### PnR Using Innovus for Modular and Behavioral Design:



Behavioral ALU  
Final Layout



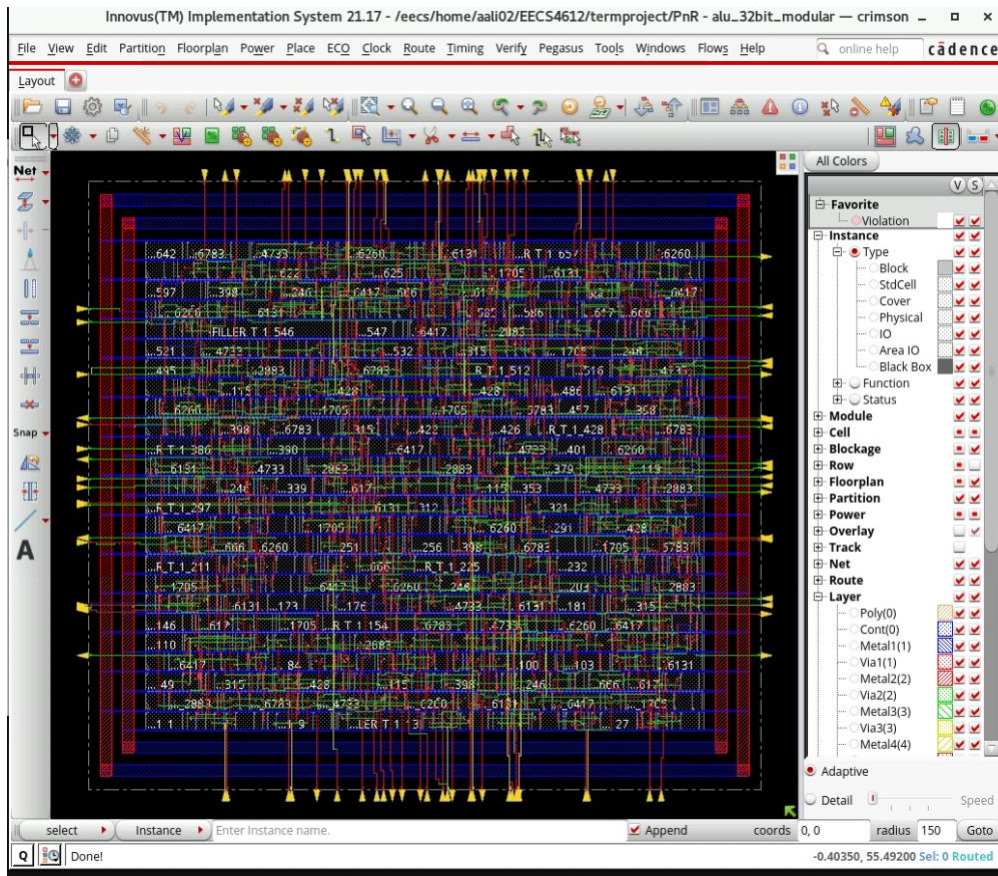

modular ALU  
Final Layout

Above we can see both screenshots of the final PnR layout with power routing, and all filler placements. This is now ready for Virtuoso. But before we do that, we need to compare both designs and pick which one will be our final. We need to do some comparison of the power, speed and area. We see this below.

Open

genus\_alu\_32bit\_modular\_power.rep  
~EECS4612/termproject/Synthesis/reports

genus\_script.tcl

Instance: /alu\_32bit\_modular  
Power Unit: W  
PDB Frames: /stim#0/frame#0

Category	Leakage	Internal	Switching	Total	Row%
memory	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
register	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
latch	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
logic	4.96023e-08	4.39078e-07	2.51057e-05	2.55943e-05	100.00%
bbox	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
clock	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
pad	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
pm	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
Subtotal	4.96023e-08	4.39078e-07	2.51057e-05	2.55943e-05	100.00%
Percentage	0.19%	1.72%	98.09%	100.00%	100.00%

Open

genus\_alu\_32bit\_modular  
~EECS4612/termproject/Synthesis/reports

genus\_script.tcl

Wireload mode: enclosed  
Area mode: timing library

Gate	Instances	Area	Library
ADDFX1	32	164.160	slow_vdd1v0
AND2XL	32	43.776	slow_vdd1v0
AND3XL	32	65.664	slow_vdd1v0
BUFEX2	31	53.010	slow_vdd1v0
BUFEX3	1	2.052	slow_vdd1v0
BUFEX6	1	3.078	slow_vdd1v0
CLKBUFEX20	33	270.864	slow_vdd1v0
CLKINX4	1	1.710	slow_vdd1v0
CLKMX2X12	32	207.936	slow_vdd1v0
INVX1	1	0.684	slow_vdd1v0
INVX1	32	21.888	slow_vdd1v0
MX2XL	96	229.824	slow_vdd1v0
MX4XL	32	229.824	slow_vdd1v0
NAND2X1	32	32.832	slow_vdd1v0
NOR2BX1	32	43.776	slow_vdd1v0
NOR2X1	32	32.832	slow_vdd1v0
NOR3BX2	1	3.420	slow_vdd1v0
OR2XL	32	43.776	slow_vdd1v0
total	485	1451.106	

Type	Instances	Area	Area %
inverter	34	24.282	1.7
buffer	66	329.004	22.7
logic	385	1097.820	75.7
physical_cells	0	0.000	0.0
total	485	1451.106	100.0

```
*alu_32bit_modular_postRoute_all.tarpt
~/EECS4612/temproject/PnR/timingReports

#####
# Generated by: Cadence Innovus 21.17-s075_1
# OS: Linux x86_64(Host ID crimson)
# Generated on: Sat Dec 13 15:09:43 2025
# Design: alu_32bit_modular
# Command: timeDesign -postRoute -pathReports -drvReports -slackReports
#####
Path 1: MET Late External Delay Assertion
Endpoint: Cout (^) checked with leading edge of 'clk'
Beginpoint: sel[1] (^) triggered by leading edge of 'clk'
Path Groups: {clk}
Analysis View: worst_case
Other End Arrival Time 0.000
- External Delay 0.030
+ Phase Shift 1000.000
= Required Time 999.970
- Arrival Time 86.157
= Slack Time 913.812
Clock Rise Edge 0.000
+ Input Delay 0.010
+ Drive Adjustment 0.112
= Beginpoint Arrival Time 0.122
#####
```

The above screenshots show the modular ALU which show an area of  $1451.105 \times 10^{-6}$  meter squared. The power is  $2.5 \times 10^{-5}$  watts. According to the timing analysis, the max frequency of this circuit is:  $1/\text{arrival time} = 11.61 \text{ mHz}$ .

Now let's compare this to the behavioral chip. After that we will compare both stats side by side.

Area mode: timing library			
Gate	Instances	Area	Library
ADDFX1	32	164.160	slow_vdd1v0
AND2X1	2	2.736	slow_vdd1v0
A021X1	32	76.608	slow_vdd1v0
A0I22X1	32	65.664	slow_vdd1v0
A0I32X1	32	76.608	slow_vdd1v0
BUF2X	32	54.720	slow_vdd1v0
CLKAND2X8	1	5.814	slow_vdd1v0
CLKBUF2X0	33	270.864	slow_vdd1v0
INVX1	35	23.940	slow_vdd1v0
MX2XL	32	76.608	slow_vdd1v0
NAND2X1	1	1.026	slow_vdd1v0
NAND2XL	32	32.832	slow_vdd1v0
NOR2BX2	1	2.736	slow_vdd1v0
NOR2X1	1	1.026	slow_vdd1v0
NOR2X4	1	3.078	slow_vdd1v0
OA21X2	1	3.078	slow_vdd1v0
OAI211X1	64	109.440	slow_vdd1v0
OR2X1	1	1.368	slow_vdd1v0
OR2X2	2	3.420	slow_vdd1v0
total	367	975.726	
Type	Instances	Area	Area %
inverter	35	23.940	2.5
buffer	65	325.584	33.4
logic	267	626.202	64.2
physical_cells	0	0.000	0.0
total	367	975.726	100.0

Category	Leakage	Internal	Switching	Total	Rov%
memory	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
register	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
latch	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
logic	3.61007e-08	3.28942e-07	2.49149e-05	2.52799e-05	100.00%
bbox	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
clock	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
pad	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
pm	0.00000e+00	0.00000e+00	0.00000e+00	0.00000e+00	0.00%
Subtotal	3.61007e-08	3.28942e-07	2.49149e-05	2.52799e-05	100.00%
Percentage	0.14%	1.30%	98.56%	100.00%	100.00%

```
alu_32bit_behavioral_postRoute_all.tarpt
~/EECS4612/temproject/PnR/timingReports

#####
# Generated by: Cadence Innovus 21.17-s075_1
# OS: Linux x86_64(Host ID crimson)
# Generated on: Sat Dec 13 15:42:28 2025
# Design: alu_32bit_behavioral
# Command: timeDesign -postRoute -pathReports -drvReports -slackReports
#####
Path 1: MET Late External Delay Assertion
Endpoint: F[31] (v) checked with leading edge of 'clk'
Beginpoint: S[0] (^) triggered by leading edge of 'clk'
Path Groups: {clk}
Analysis View: worst_case
Other End Arrival Time 0.000
- External Delay 0.030
+ Phase Shift 1000.000
= Required Time 999.970
- Arrival Time 61.008
= Slack Time 938.962
Clock Rise Edge 0.000
+ Input Delay 0.010
+ Drive Adjustment 0.059
= Beginpoint Arrival Time 0.069
#####
```

The max frequency can be calculated using  $1/\text{arrival time} = 16.39 \text{ MHz}$ .

Metric	Modular ALU	Behavioral ALU
Area	1451.106	975.726
Power	2.55 x 10 ^-5	2.52 x 10 ^ -5
Max Frequency	11.61 MHZ	16.39 MHZ

### DRC and Connectivity for Both ALUs:

The image displays two side-by-side terminal windows from the Cadence Innovus software. The left window shows the command prompt 'innovus > VERIFY\_CONNECTIVITY use new engine.' and the subsequent output of the 'verify\_connectivity' command. The output includes design information (Design Name: alu\_32bit\_behavioral, Database Units: 2000, Design Boundary: {0.0000, 0.0000} (50.8000, 44.4600), Error Limit = 1000; Warning Limit = 50), a summary of the verification process (Found no problems or warnings), and the final completion message (Verification Complete : 0 Viols. 0 Wrngs. (CPU Time: 0:00:00.0 MEM: 0.000M)). The right window shows the same command prompt, but the output is truncated, showing only the initial part of the verification process (Starting Verification, Initializing, Deleting Existing Violations, Creating Sub-Areas, Using new threading, Sub-Area: {0.000 0.000 50.800 44.460} 1 of 1, Sub-Area : 1 complete 0 Viols.) and the final completion message (Verification Complete : 0 Viols.).

```
crimson:/eecs/home/aali02/EEC54612/termproject/PnR
File Edit View Search Terminal Tabs Help

crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...

VERIFY DRC ..... Using new threading
VERIFY DRC ..... Sub-Area: {0.000 0.000 50.800 44.460} 1 of 1
VERIFY DRC ..... Sub-Area : 1 complete 0 Viols.

Verification Complete : 0 Viols.

*** End Verify DRC (CPU: 0:00:00.0 ELAPSED TIME: 0.00 MEM: 256.1M) ***

innovus > VERIFY_CONNECTIVITY use new engine.

***** Start: VERIFY CONNECTIVITY *****
Start Time: Sat Dec 13 15:41:31 2025

Design Name: alu_32bit_behavioral
Database Units: 2000
Design Boundary: {0.0000, 0.0000} (50.8000, 44.4600)
Error Limit = 1000; Warning Limit = 50
Check all nets

Begin Summary
  Found no problems or warnings.
End Summary

End Time: Sat Dec 13 15:41:31 2025
Time Elapsed: 0:00:00.0

***** End: VERIFY CONNECTIVITY *****
Verification Complete : 0 Viols. 0 Wrngs.
(CPU Time: 0:00:00.0 MEM: 0.000M)

innovus >

crimson:/eecs/home/aali02/EEC54612/termproject/PnR
File Edit View Search Terminal Tabs Help

crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...  crimson:/eecs/home/aali02/EEC54612/ter...

innovus > **WARN: (IMPSP-5217):
d by ecoRoute -target command to make the DRC clean.
type 'man IMPSP-5217' for more detail.
*INFO: Adding fillers to top-module.
*INFO: Added 0 filler inst (cell FILL64 / prefix FILLER).
*INFO: Added 1 filler inst (cell FILL32 / prefix FILLER).
*INFO: Added 15 filler insts (cell FILL16 / prefix FILLER).
*INFO: Added 96 filler insts (cell FILL8 / prefix FILLER).
*INFO: Added 172 filler insts (cell FILL4 / prefix FILLER).
*INFO: Added 145 filler insts (cell FILL2 / prefix FILLER).
*INFO: Added 161 filler insts (cell FILL1 / prefix FILLER).
*INFO: Total 590 filler insts added - prefix FILLER (CPU: 0:00:00.1).
For 590 new insts, innovus > #-check_ndr spacing auto # enums={true false auto}, default=auto, user setting
#-check same via cell true # bool, default=false, user setting
#-exclude pg net true # bool, default=false, user setting
#-report alu_32bit_behavioral.drc.rpt # string, default="", user setting
*** Starting Verify DRC (MEM: 2676.5) ***


VERIFY DRC ..... Starting Verification
VERIFY DRC ..... Initializing
VERIFY DRC ..... Deleting Existing Violations
VERIFY DRC ..... Creating Sub-Areas
VERIFY DRC ..... Using new threading
VERIFY DRC ..... Sub-Area: {0.000 0.000 50.800 44.460} 1 of 1
VERIFY DRC ..... Sub-Area : 1 complete 0 Viols.

Verification Complete : 0 Viols.

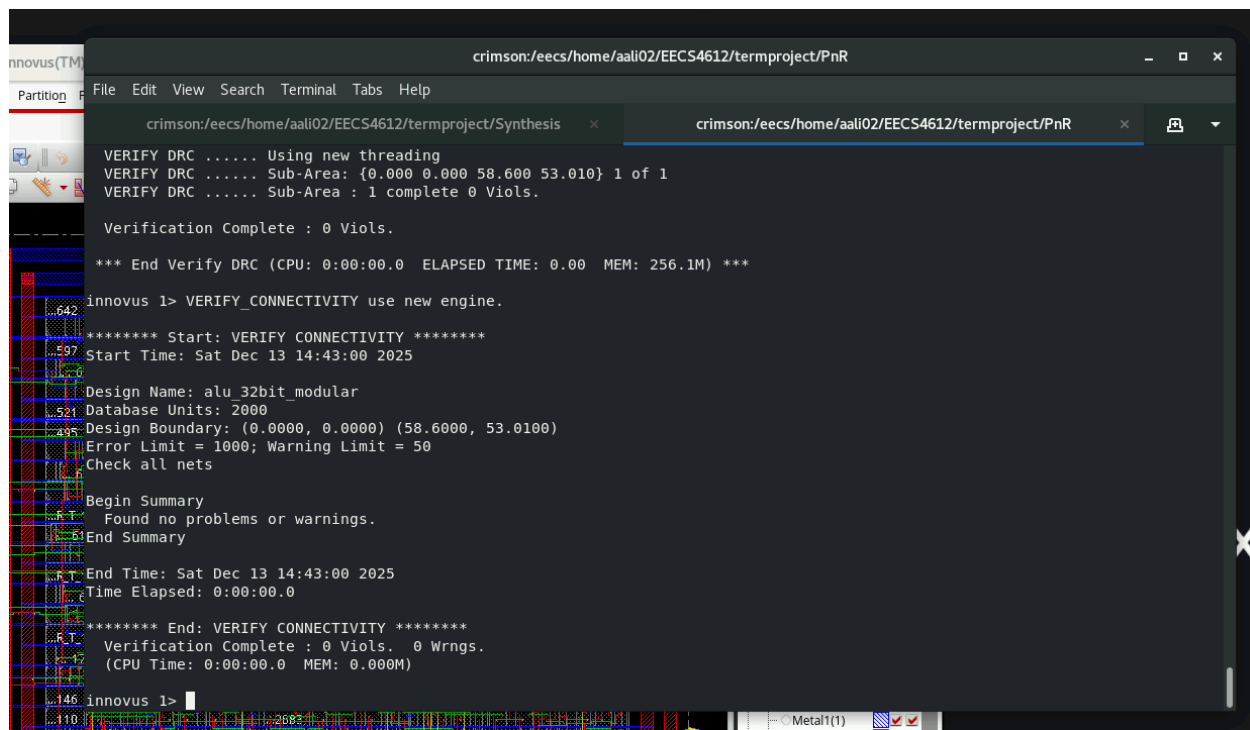*** End Verify DRC (CPU: 0:00:00.0 ELAPSED TIME: 0.00 MEM: 256.1M) ***

innovus >
```

This is the DRC and connectivity for the **behavioral** ALU. Both checks passed with 0 violations.



```
crimson:/eecs/home/aali02/EECS4612/termproject/PnR
File Edit View Search Terminal Tabs Help

crimson:/eecs/home/aali02/EECS4612/termproject/Synthesis x crimson:/eecs/home/aali02/EECS4612/termproject/PnR x

VERIFY DRC ..... Using new threading
VERIFY DRC ..... Sub-Area: {0.000 0.000 58.600 53.010} 1 of 1
VERIFY DRC ..... Sub-Area : 1 complete 0 Viols.

Verification Complete : 0 Viols.

*** End Verify DRC (CPU: 0:00:00.0 ELAPSED TIME: 0.00 MEM: 256.1M) ***

innovus 1> VERIFY_CONNECTIVITY use new engine.
***** Start: VERIFY CONNECTIVITY *****
Start Time: Sat Dec 13 14:43:00 2025


Design Name: alu_32bit_modular
Database Units: 2000
Design Boundary: (0.0000, 0.0000) (58.6000, 53.0100)
Error Limit = 1000; Warning Limit = 50
Check all nets

Begin Summary
Found no problems or warnings.
End Summary

End Time: Sat Dec 13 14:43:00 2025
Time Elapsed: 0:00:00.0

***** End: VERIFY CONNECTIVITY *****
Verification Complete : 0 Viols. 0 Wrngs.
(CPU Time: 0:00:00.0 MEM: 0.000M)

innovus 1>
```

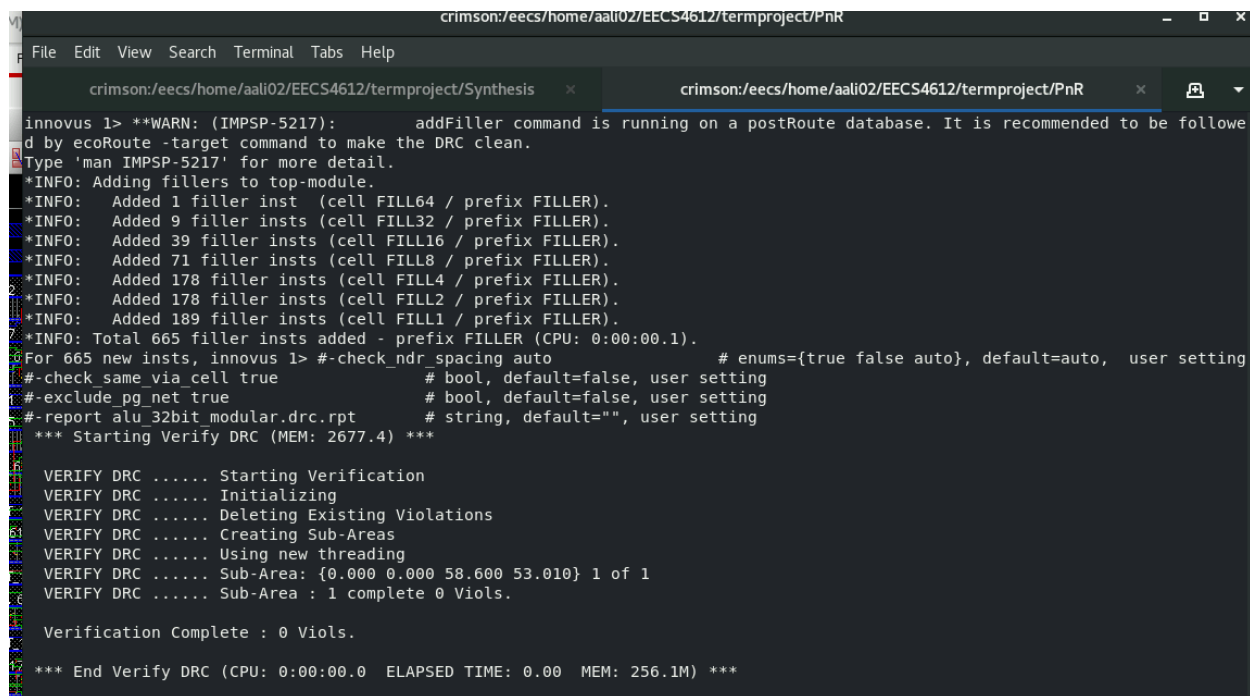

```
crimson:/eecs/home/aali02/EECS4612/termproject/PnR
File Edit View Search Terminal Tabs Help

crimson:/eecs/home/aali02/EECS4612/termproject/Synthesis x crimson:/eecs/home/aali02/EECS4612/termproject/PnR x

innovus 1> **WARN: (IMPSP-5217): addFiller command is running on a postRoute database. It is recommended to be followe
d by ecoRoute -target command to make the DRC clean.
Type 'man IMPSP-5217' for more detail.
*INFO: Adding fillers to top-module.
*INFO: Added 1 filler inst (cell FILL64 / prefix FILLER).
*INFO: Added 9 filler insts (cell FILL32 / prefix FILLER).
*INFO: Added 39 filler insts (cell FILL16 / prefix FILLER).
*INFO: Added 71 filler insts (cell FILL8 / prefix FILLER).
*INFO: Added 178 filler insts (cell FILL4 / prefix FILLER).
*INFO: Added 178 filler insts (cell FILL2 / prefix FILLER).
*INFO: Added 189 filler insts (cell FILL1 / prefix FILLER).
*INFO: Total 665 filler insts added - prefix FILLER (CPU: 0:00:00.1).
For 665 new insts, innovus 1> #-check_ndr_spacing auto # enums={true false auto}, default=auto, user setting
#-check_same_via_cell true # bool, default=false, user setting
#-exclude_pg_net true # bool, default=false, user setting
#-report alu_32bit_modular.drc.rpt # string, default="", user setting
*** Starting Verify DRC (MEM: 2677.4) ***

VERIFY DRC ..... Starting Verification
VERIFY DRC ..... Initializing
VERIFY DRC ..... Deleting Existing Violations
VERIFY DRC ..... Creating Sub-Areas
VERIFY DRC ..... Using new threading
VERIFY DRC ..... Sub-Area: {0.000 0.000 58.600 53.010} 1 of 1
VERIFY DRC ..... Sub-Area : 1 complete 0 Viols.

Verification Complete : 0 Viols.


*** End Verify DRC (CPU: 0:00:00.0 ELAPSED TIME: 0.00 MEM: 256.1M) ***
```

The above screenshots show the DRC and connectivity for the **modular** ALU. For this one the checks passed as well with 0 violations.


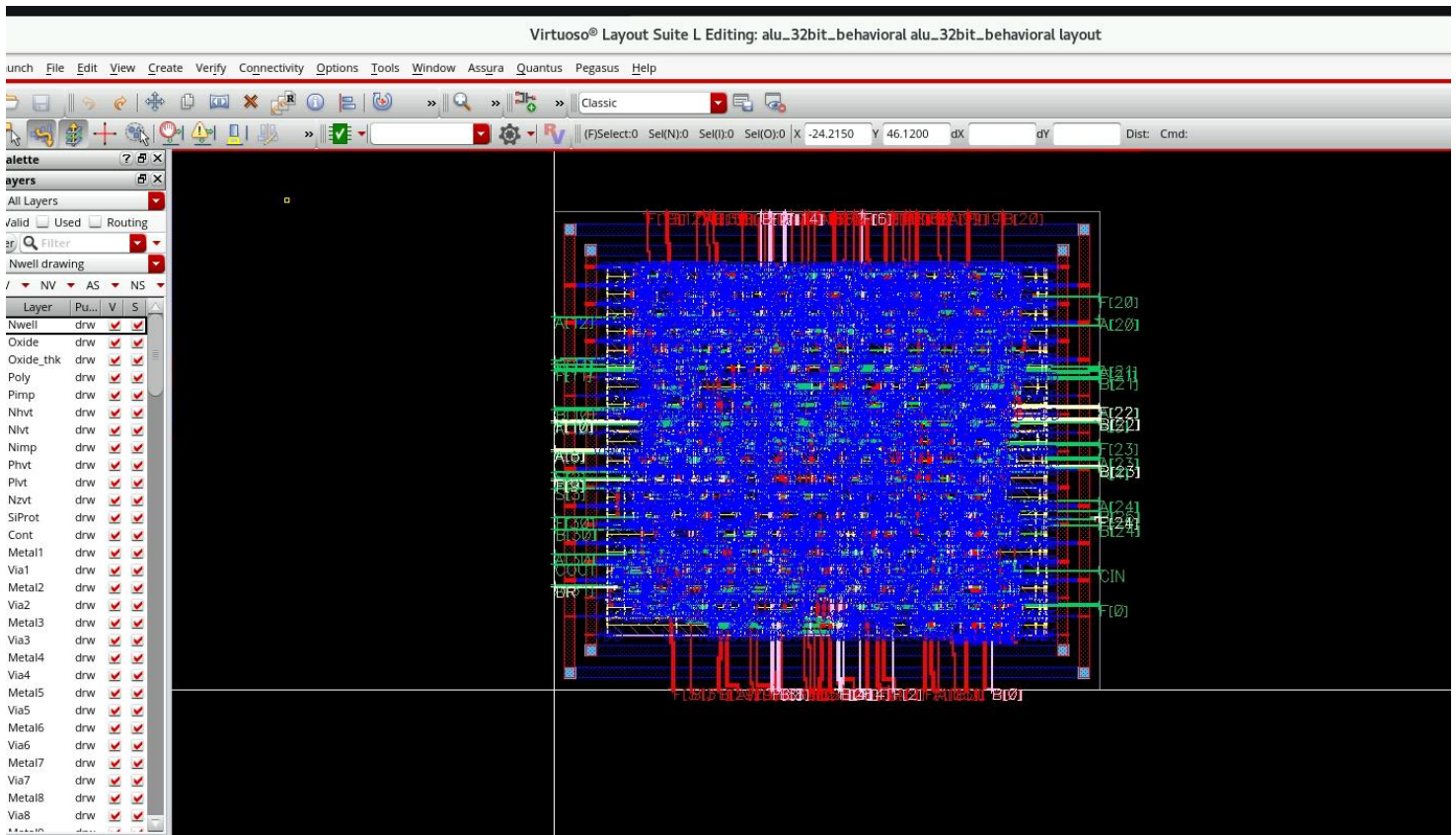
## Exporting Final Design

Now that we have decided to move along with the behavioral ALU as our final design, that is the one that we are going to attach to the padframe. The other GDS file for the modular ALU has been uploaded to eClass.



Above is a picture of the final integrated layout of the 32-bit ALU behavioral. This will now be integrated within the padframe.



The very last step is the timing analysis. Even though the measurements were conducted, the timing will be the same as the behavioral. We calculate it using the formula  $f_{max} = \frac{1}{criticalpathdelay}$ . So, this comes out to be  $1/61.008 \times 10^{-9} = 16.39$  MHZ. So, we can conclude that the maximum speed for this 32-bit ALU is 16.39 MHZ.